

Ch 7

Sec 7.3A

obj: How does a transformer change the voltage of an alternating current?

Transformer

- Two separate coils that are wrapped around a single core.
- \* Primary Coil - Connected to an AC source
- \* Secondary Coil - Connected to an external circuit.
- The primary and secondary coils are not connected.
- The purpose of a transformer is to change AC Voltage.

Step-Up + Step Down Transformers


- Step-Up Voltage Transformer increases the voltage from the primary coil.
  - \* The number of turns in the secondary coil is greater than that in the primary coil.
  - \* Turns ratio is used to determine how the voltage changes.
- $$\text{Turns Ratio} = \frac{\# \text{Turns Secondary}}{\# \text{Turns Primary}}$$
- \* The turns ratio is a multiplier of the primary voltage.

$$\begin{aligned} \# \text{Turns Secondary} &= 100 \\ \# \text{Turns Primary} &= 50 \\ \text{Turns Ratio} &= \frac{100}{50} \\ &= 2 \end{aligned}$$

- Stepdown Voltage Transformer

- \* Reduces the voltage from the primary coil.
- \* # of turns in the primary coil is greater than that in the secondary coil.
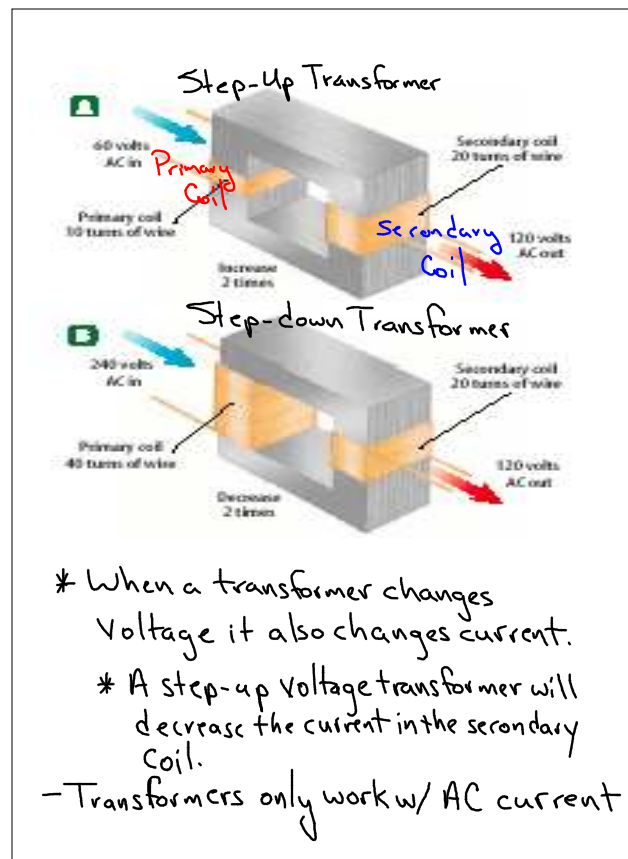
$$\begin{aligned} \# \text{Turns in Secondary} &= 25 \\ \# \text{Turns in Primary} &= 100 \\ \text{Turns Ratio} &= \frac{25}{100} = .25 \end{aligned}$$



- Transformers only work w/ an AC

